

Roll No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 07

**BCA (2013 & Onward) (Sem.-3)**  
**DIGITAL CIRCUITS AND LOGIC DESIGN**  
Subject Code : BSBC-303  
Paper ID : [B0230]

Time : 3 Hrs.

Max. Marks : 60

**INSTRUCTION TO CANDIDATES :**

1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
2. SECTION-B contains SIX questions carrying TEN marks each and a student has to attempt any FOUR questions.

**SECTION-A**

**Q1) Answer briefly :**

- a) What are universal gates?
- b) Draw circuit of full adder with truth table.
- c) What are the steps of removing race condition?
- d) Write a short note on decoder.
- e) What are combinational circuits?
- f) Convert  $(274)_{10} = (?)_2$ .
- g) What is a latch?
- h) What is parallel binary adder?
- i) Write a short note on D flip flop.
- j) What is the use of K maps?

## SECTION-B

- Q2) Explain half adder and full adder in detail.
- Q3) What are multiplexers? Design and explain the working of 16 to 1 line multiplexer.
- Q4) Discuss flip flops. What are its different types and applications?
- Q5) Explain the internal architecture of 555 timer in detail.
- Q6) What is number system? Explain 1's complement and 2's complement with example.
- Q7) Write a short note on Encoders. Discuss their applications. Design an 8- Input Priority Encoder using basic gates.