	Roll No												
--	---------	--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 09

# B.Sc. Honours (Physics) (Sem.–3) ANALOG SYSTEMS AND APPLICATION Subject Code : BSHP-214-21 M.Code : 92457 Date of Examination : 16-12-22

Time: 3 Hrs.

Max. Marks : 60

# INSTRUCTIONS TO CANDIDATES :

- 1. SECTION-A is COMPULSORY consisting of TEN questions carrying TWO marks each.
- 2. SECTION B & C. have FOUR questions each.
- 3. Attempt any FIVE questions from SECTION B & C carrying EIGHT marks each.
- 4. Select atleast TWO questions from SECTION B & C.

### **SECTION-A**

### **l.** Write short notes on :

- a) Define Mobility and discuss the factor on which mobility depends.
- b) Discuss the effect of forward and reverse bias on contact potential.
- c) What is the use of C-filter in rectifiers?
- d) What is Q-point in bipolar junction transistors?
- e) Calculate the wavelength of light emitted from a LED made up of material with band gap 1.24 eV.
- f) Define hybrid parameters for transistor.
- g) Write a note on Class B amplifiers.
- h) What is Barkhausen criterion?
- i) What is the use tank circuit in oscillators?
- j) The tuned collector circuit use an LC tuned circuit with  $L = 58.6 \mu H$  and C = 300 pF. Calculate the frequency of oscillator.

#### **SECTION-B**

- 2. Drive the expression for barrier potential of a p-n junction.
- 3. What is a Zener diode? Discuss its operation as voltage regulator.
- 4. Draw a neat diagram to study the V-I characteristics for forward and reverse biased diode and discuss various features of V-I characteristics.
- 5. Explain the mechanism of a amplification in a transistor. Show that output signal is in phase with input signal in common base confirmation.

### SECTION-C

- 6. Draw a fixed bias circuit and obtain the expression for its stability factor.
- 7. Find the values of current gain and voltage gain for a small signal common collector amplifier.
- 8. Draw the circuit diagram of a Tunes collector oscillator and determine the condition for sustained oscillations.
- 9. Explain the principle and working of a RC phase shift oscillator with help of a neat circuit diagram.

NOTE : Disclosure of Identity by writing Mobile No. or Marking of passing request on any paper of Answer Sheet will lead to UMC against the Student.