

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 18

B.Tech (CSE/IT) (Sem.-3)
DIGITAL CIRCUITS & LOGIC DESIGN
Subject Code : BTCS-303
Paper ID : [A1125]

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

SECTION-A

Answer briefly :

- Q1. Compare combinational with sequential circuits?
- Q2. What is the use of parity checker?
- Q3. What are Karnaugh Maps?
- Q4. Draw a 4*1 multiplexer?
- Q5. Write the truth table of JK Flip Flop?
- Q6. Draw *T* type of Flip Flop?
- Q7. Define edge triggering?
- Q8. Discuss read operation in memory?
- Q9. What is static RAM cell?
- Q10. What is Moore circuit?

SECTION-B

- Q11. What are weighted and non weighted codes?
- Q12. Design a combination circuits for a full adder and explain it in detail?
- Q13. What are shift registers? Explain the shift right operation?
- Q14. What is Field Programmable Gate Arrays (FPGAs) and how it is used?
- Q15. Explain the principle operation of RTL & DTL?

SECTION-C

- Q16. Discuss principle of duality in De-Morgan Theorem. Explain minimization of Boolean expression using SOP by taking an example?
- Q17. Explain Ripple counter and draw its logic diagram and timing diagram?
- Q18. What are the types of digital to analog converter techniques? Explain R-2R ladder in detail?