

Roll No.									
----------	--	--	--	--	--	--	--	--	--

**Total No. of Pages : 02**

**Total No. of Questions : 09**

**B.Tech. (Artificial Intelligence (AI) and Data Science / CSE / (CSE)(AI&ML) /(CSE)(Data Science) /(CSE)(IOT)/(Data Science)/ IT / CSE (Internet of Things and Cyber Security including Block Chain Technology)) (Sem.-3)**

# DIGITAL ELECTRONICS

**Subject Code : BTES301-18**

**M.Code : 76435**

**Date of Examination : 24-05-2023**

Time : 3 Hrs.

**Max. Marks : 60**

**INSTRUCTIONS TO CANDIDATES :**

1. **SECTION-A is COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

## SECTION-A

**1. Write briefly :**

- What is the need of digital electronics? Discuss.
- List the various disadvantages of Boolean algebra.
- Differentiate between combinational and sequential circuits.
- What is the need of a flip flop? Discuss.
- What do you mean by MUX? Discuss.
- What do you mean by excitation table? Discuss.
- What do you mean by race around condition? Discuss.
- Discuss the significance of D flip-flop.
- Write down the need of sample and hold circuit.
- What do you mean by memory cycle? Discuss.

## SECTION-B

2. Implement the half adder using :
  - a) AOI
  - b) NAND gates only .
3. In an industry four operations Temperature, Pressure, Level and Humidity are to be encoded. Design a priority encoder in which Temperature must have the highest priority then Pressure followed by Level and Humidity is having the lowest priority.
4. Explain the working of a JK flip-flop. Also, discuss how the problem of SR flip flop is solved in JK flip flop?
5. Draw the diagram and discuss the working of R-2R type D/A converter in detail.
6. Explain the ROM organization and its comparison with RAM.

## SECTION-C

7. Draw and explain the working of Successive approximation and dual slope A/D converters.
8. a) Reduce the following expression to simplest form using K map method  $F(A,B,C,D) = \sum m (0,2,5,6,7,10,11,12)$ 
  - b) Draw the logical diagram and explain the working of BCD adder.
9. Explain :
  - a) FPGA
  - b) Gray and Excess 3 codes

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**