

Roll No. 

--	--	--	--	--	--	--	--	--	--	--	--

Total No. of Pages : 02

Total No. of Questions : 18

**B.Tech.(CSE)/(IT) (2012 to 2017) (Sem.-3)**

**DIGITAL CIRCUITS & LOGIC DESIGN**

**Subject Code : BTCS-303**

**M.Code : 56593**

**Time : 3 Hrs.**

**Max. Marks : 60**

**INSTRUCTIONS TO CANDIDATES :**

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

**SECTION-A**

**Write Briefly :**

1. Convert a D flip flop into T flip flop
2. Design a 4:1 MUX
3. Parity Checker
4. MOSFET RAM
5. Function of Multivibrator
6. RTL versus DCTL
7. Convert  $11001_2$  to decimal
8. What is resolution in A/D Converter?
9. Find the state diagram to design a sequence detector circuit, which detects three or more consecutive 1's in a string of bits coming through an input line.
10. EEPROM

### SECTION-B

11. Design full subtractor using De-Multiplexer.
12. Using Boolean algebra show that :
$$AB + \overline{A}C + BC = AB + \overline{A}C$$
13. Explain the structure of typical RAM cell.
14. Draw and explain logic diagram of a mod-8 ripple counter using three JK flipflops.
15. What is difference in 1's and 2's Complement? Which of two is better to represent negative numbers? Why?

### SECTION-C

16. What are the different A/D and D/A conversion techniques? Explain in detail.
17. What do you understand by Boolean expressions and need of their minimization? Elaborate SOP and POS.
18.
  - a. Draw a truth table for 4-input 'OR' Gate and 3-input 'NAND' Gate
  - b. Define Interfacing and show the interfacing of two TTL gates. Also discuss their characteristics.

**NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.**