

Roll No.

Total No. of Pages : 02

Total No. of Questions : 09

B.Tech.(ME) (Sem.-3)

BASIC ELECTRONICS ENGINEERING

Subject Code : BTEC305-18

M.Code : 76420

Date of Examination: 26-05-2023

Time : 3 Hrs.

Max. Marks : 60

INSTRUCTIONS TO CANDIDATES :

1. **SECTION-A** is **COMPULSORY** consisting of **TEN** questions carrying **TWO** marks each.
2. **SECTION-B** contains **FIVE** questions carrying **FIVE** marks each and students have to attempt any **FOUR** questions.
3. **SECTION-C** contains **THREE** questions carrying **TEN** marks each and students have to attempt any **TWO** questions.

SECTION-A

1. Write Briefly :

- a) What is peak inverse voltage?
- b) What is breakdown voltage?
- c) What are filter circuits?
- d) What is center tap full wave rectifier?
- e) What is meant by LSB and MSB.
- f) What is photo diode? Which material is used for them?
- g) What is operating point?
- h) What is comparator?
- i) What is the truth table of NAND and NOR gate?
- j) Convert the hexadecimal number into octal:
 - i. 5B.34
 - ii. 3DE

SECTION-B

2. Explain the working of full wave rectifier with filtered output.
3. Draw and explain the three basic configurations of NPN transistor.
4. Explain with diagram how an op-amp can be used as phase shifter.
5. Explain JK flip flop with its truth table.
6. Solve the following :

a) $(5735.20)_8 = (?)_2 = (?)_{16}$

b) $(A152)_{16} = (?)_8 = (?)_2$

c) Add $(100000.001)_2 = (11110.111)_2$

SECTION-C

7. Explain the block diagram of an operational amplifier? Also draw the pin diagram of 741 op-amp.
8. Explain the working of an Emitter Follower and show how it performs the function of impedance transformation.
9. **Write short note on the following :**
 - a) SR Flip flop
 - b) Common mode rejection ratio and slew rate in op-amp

NOTE : Disclosure of Identity by writing Mobile No. or Making of passing request on any page of Answer Sheet will lead to UMC against the Student.